

25 Spring ECEN 610: Mixed-Signal Interfaces

Lab3: Analysis and Simulation of switched Gm-C Filters

Name: Yu-Hao Chen

UIN:435009528

Section:601

Professor: Sebastian Hoyos

TA: Sky Zhao


https://github.com/Yu-HaoChen/TAMU_ECEN610_Mixed_signal/tree/main

- Consider the following circuit, where $N=8$ and the frequency of the clocks is 2.4 GHz and $C_s=15.925$ pF. The capacitors are charged in a cyclic fashion by the input current i_{RF} . Similarly, the voltage stored in the capacitors C_s is read cyclically at the end of each consecutive N cycles. The output of the circuit is the concatenation of the cyclic readings of the voltages. Consider the following 2 cases:

- The capacitors are discharged after each read out operation, i.e. the charge of the capacitors is zero at the beginning of the integration of every N cycles.
- The capacitors are never discharged.

In both cases find the filter transfer function $H(f)=V_o(f)/i_{RF}(f)$ where $V_o(f)$ is the capacitor voltage. Please use a mathematical description of how the transfer function is found and then use Python to plot the transfer functions.

$$H(f) = \frac{V_o(f)}{i_{RF}(f)}$$

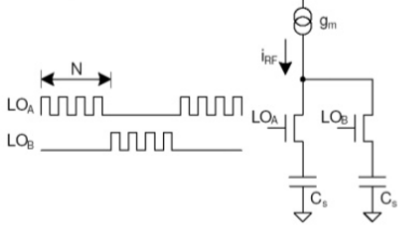

$$T_{LO} = \frac{1}{2.4G} \approx 0.4167 \text{ ns}$$

$$0.4167 \text{ ns} \times 8 = 3.33 \text{ ns}$$

$$V_{Cs}(t) = \frac{1}{C} \int_0^t i_{RF}(\tau) d\tau \quad 0 \leq t \leq T_{int}$$

$$w(t) = \begin{cases} 1, & 0 \leq t \leq T_{int} \\ 0, & \text{other} \end{cases}$$

$$W(f) = \int_{-\infty}^{\infty} w(t) e^{-j2\pi ft} dt$$


$$w(f) = \int_0^{T_{int}} 1 \times e^{-j2\pi ft} dt$$

$$= \left. \frac{e^{-j2\pi ft}}{-j2\pi f} \right|_{t=0}^{t=T_{int}}$$

$$= \frac{1}{-j2\pi f} (e^{-j2\pi f T_{int}} - 1)$$

$$= \frac{1 - e^{-j2\pi f T_{int}}}{j2\pi f}$$

Fourier

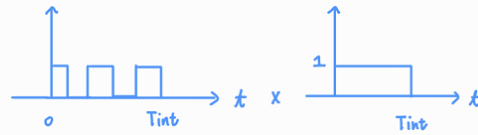


$$X(t) \times w(t)$$

$$\updownarrow$$

$$X(f) * w(f)$$
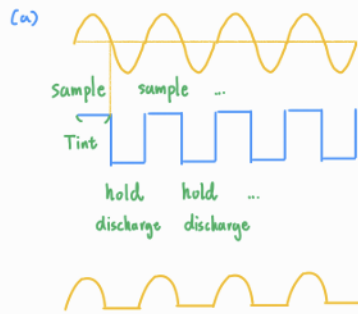
$$V_o = H(f) \times \frac{1}{C} \times i_{RF}$$




$$\lim_{f \rightarrow 0} \frac{1 - e^{-j2\pi f T_{int}}}{j2\pi f} = T_{int}$$

$$V_C(t) = \frac{1}{C} \int_0^t i_{RF}(\tau) d\tau \quad 0 \leq t \leq T_{int}$$

$$H_a(f) = \frac{1}{C} \left(\frac{1 - e^{-j2\pi f T_{int}}}{j2\pi f} \right) \left(\frac{1 - e^{-j2\pi f T_{int}}}{j2\pi f \times T_{int}} \right)$$

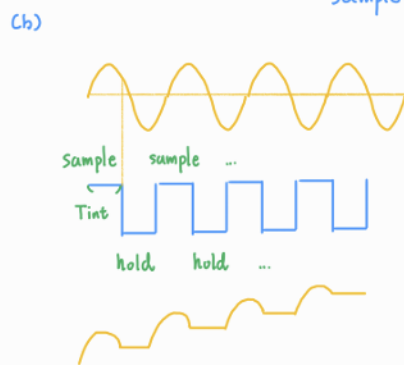
sample hold (V not change $\rightarrow f=0$)




$$V_C(t) = \frac{1}{C} \int_0^t i_{RF}(\tau) d\tau \quad t \geq 0$$

$$H_b(f) = \frac{1}{C} \left(\frac{1}{j2\pi f} \right) \left(\frac{1 - e^{-j2\pi f T_{int}}}{j2\pi f \times T_{int}} \right)$$

intergrated hold

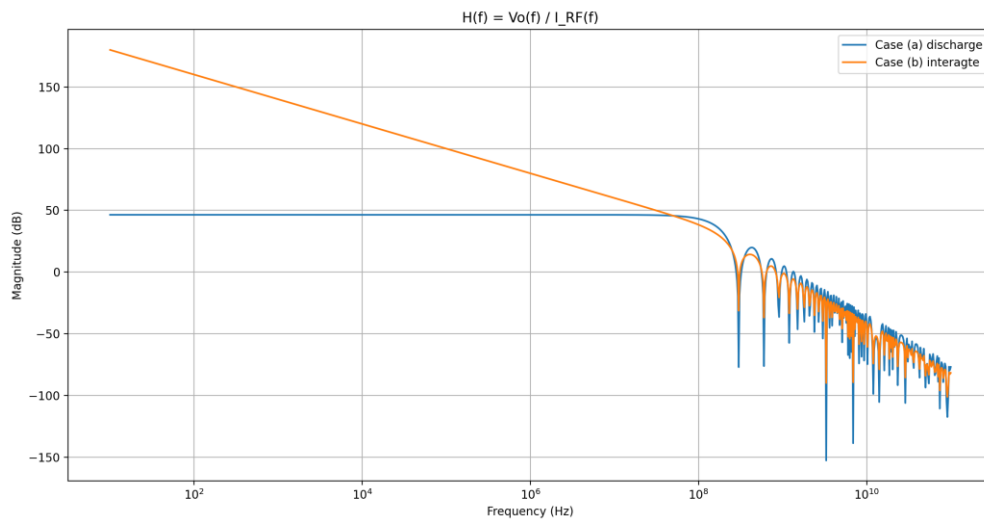

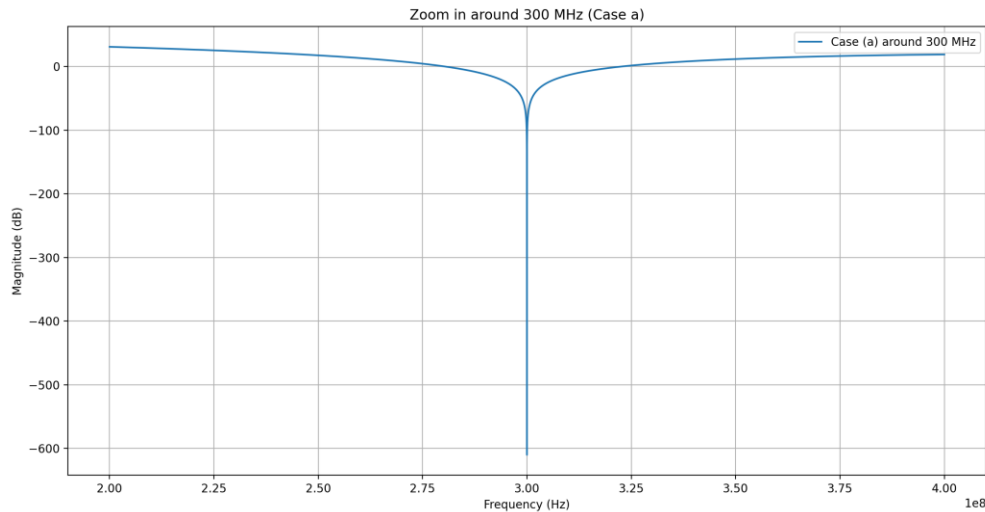

According to model as moving average, the filter has a sinc frequency response with null positions at $k \cdot f_0 / N = k \cdot 300 \text{M}$ where $k=1,2,3\dots$ (clear o discharge at every $T \cdot n$ period, in freq gain=0)

Case (a): Since the integrator resets (dumping the accumulated charge) at each interval, it only averages the input over that short time period. For very low-frequency signals (even DC), the output is limited to this brief average and then reset, resulting in a lower and flatter response.

Case (b): The integrator never resets, so the capacitor continuously accumulates charge. This continuous integration allows the output for very low-frequency signals (and DC) to build up over time, yielding a higher response at low frequencies compared to case (a).


2. Now consider the addition of a “history” capacitor $C_H=15.425 \text{ pF}$ and a “rotating” capacitor $C_R=0.5 \text{ pF}$.
 - a.) Explain the effect of adding the capacitor C_H in the transfer function that was calculated in problem 1.
 - b.) Find the new transfer function and plot it using Python.


$$s_j = a_1 s_{j-1} + w_j$$


For charge $C_s = C_H + C_R$

$$CR \text{ (periodic discharge)} = \frac{1 - e^{-j\omega T_{int}}}{j\omega f C_s}$$

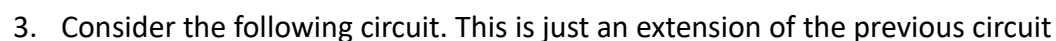Transfer Function with History Capacitor C_H and Rotating Capacitor C_R



where the cyclic operation is extended to 8 capacitors. As in the previous circuit, every capacitor also stores $N=8$ cycles of the input switched current. The output voltage is defined as the voltage resulting from the physical connection of the bank of 4 capacitors enclosed by the rectangle in the figure. This read out operation is also made in a cyclic fashion between the 2 bank of capacitors. Assume ideal transistors and an ideal transconductance g_m . Find a mathematical expression for the transfer function and plot in Python for the following 2 situations.

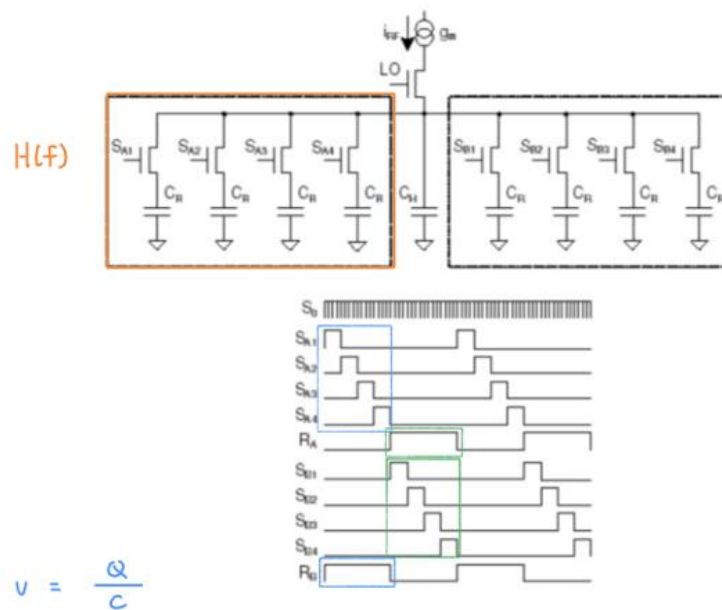

$$V = \frac{Q}{C}$$


$$(a) \quad H(f) = \frac{1}{CR} \left(\frac{1 - e^{-j2\pi f T_{int}}}{j2\pi f} \right) \left(\frac{1 - e^{-j2\pi f T_{int}}}{j2\pi f} \right)$$

(single CR) sample hold

$$V_{out} = \frac{Q_1 + Q_2 + Q_3 + Q_4}{CR_1 + CR_2 + CR_3 + CR_4}$$

assume CR are all same $\rightarrow \frac{Q}{CR}$ same with one CR

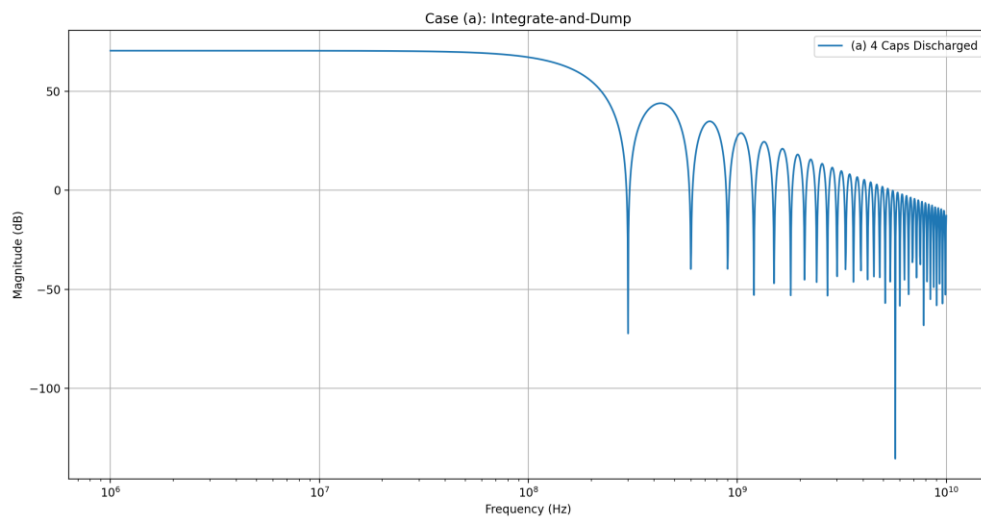
- a) The 4 capacitors are discharged after their connection and read out operation, i.e. the charge of the capacitors is zero at the beginning of the integration of every N cycles.



b) The capacitors are never discharged.

$$(b) \quad H(f) = \frac{1}{CR} \left(\frac{1}{j2\pi f} \right) \left(\frac{1 - e^{-j2\pi f T_{int}}}{j2\pi f T_{int}} \right)$$

(single CR)

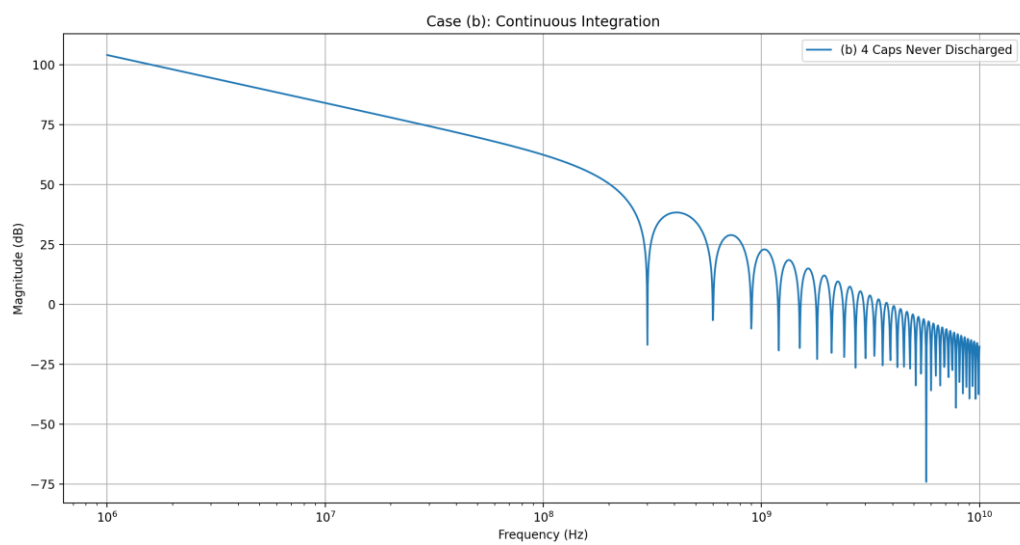

c) The capacitors are discharged but they have different sizes, i.e. CR1, CR2, CR3, CR4.


$$C(c) \quad V_{ci}(f) = \frac{1}{CR} \left(\frac{1 - e^{-j2\pi f T_{int}}}{j2\pi f} \right) \left(\frac{1 - e^{-j2\pi f T_{int}}}{j2\pi f T_{int}} \right)$$

$$V_{out} = \frac{\alpha_1 + \alpha_2 + \alpha_3 + \alpha_4}{CR_1 + CR_2 + CR_3 + CR_4} = \frac{CR_1 V_{c1} + CR_2 V_{c2} + CR_3 V_{c3} + CR_4 V_{c4}}{CR_1 + CR_2 + CR_3 + CR_4}$$

(average)

$$H(f) = \frac{4}{\sum_{i=1}^4 CR_i} \left[\frac{1 - e^{-j2\pi f T_{int}}}{j2\pi f} \right] \times \left(\frac{1 - e^{-j2\pi f T_{int}}}{j2\pi f T_{int}} \right)$$

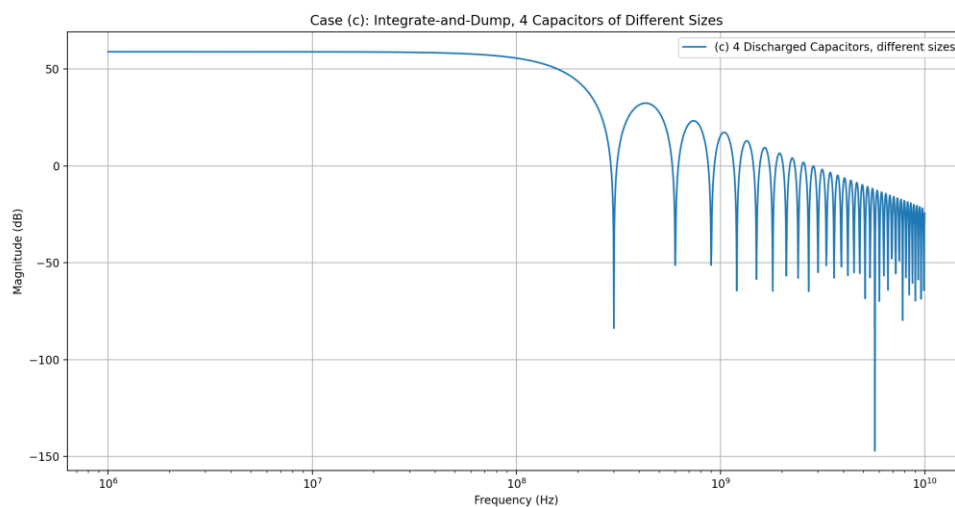$C1 = 2p \quad C2 = 3p \quad C3 = 4p \quad C4 = 6p$



Appendix

Q1

```

lab3-1.py > ...
1  import numpy as np
2  import matplotlib.pyplot as plt
3
4  # 参数设定
5  C = 15.925e-12 # 电容值 (F)
6  f_LO = 2.4e9 # LO 频率 (Hz)
7  N = 8
8  T_int = N / f_LO # 积分时间 (s)
9
10 # 频率扫描范围: 从 10Hz ~ 100 GHz
11 f = np.logspace(np.log10(10), np.log10(1e11), 1000)
12
13 w = 2 * np.pi * f
14
15 # (a) 每次读出后放电
16 H_a(f) = (1/C) * [(1 - e^(-j w T_int)) / (j w)] * [(1 - e^(-j w T_int)) / (j w T_int)]
17 Hw_a_num = (1 - np.exp(-1j * w * T_int)) # 分子 1 - e^(-j w T_int)
18 Hw_a_int = Hw_a_num / (1j * w) # 有限积分
19 Hw_a_hold = Hw_a_num / (1j * w * T_int) # ZOH
20 H_a = (1/C) * Hw_a_int * Hw_a_hold
21
22 # (b) 从不放电
23 H_b(f) = (1/C) * [1/(j w)] * [(1 - e^(-j w T_int)) / (j w T_int)]
24 Hw_b_int = 1 / (1j * w) # 连续积分 1/(j w)
25 Hw_b_hold = Hw_a_num / (1j * w * T_int) # ZOH (同上)
26 H_b = (1/C) * Hw_b_int * Hw_b_hold
27
28 # 转成绝对值 (dB)
29 H_a_mag_db = 20 * np.log10(np.abs(H_a))
30 H_b_mag_db = 20 * np.log10(np.abs(H_b))

```


Q1_check

```
lab3-1_check.py > ...
1 import numpy as np
2 import matplotlib.pyplot as plt
3
4 C = 15.925e-12
5 f_LO = 2.4e9
6 N = 8
7 T_int = N / f_LO
8
9 # 針對 200 MHz ~ 400 MHz 之間做高解析度掃描 (線性分佈)
10 f_lin = np.linspace(2.0e8, 4.0e8, 20001) # 2萬個點
11 w_lin = 2 * np.pi * f_lin
12
13 Hw_a_num = (1 - np.exp(-1j * w_lin * T_int))
14 Hw_a_int = Hw_a_num / (1j * w_lin)
15 Hw_a_hold = Hw_a_num / (1j * w_lin * T_int)
16 H_a = (1/C) * Hw_a_int * Hw_a_hold
17
18 H_a_mag_dB = 20 * np.log10(np.abs(H_a))
```

Q2

```
lab3-2.py > ...
1 import numpy as np
2 import matplotlib.pyplot as plt
3
4 CH = 15.425e-12
5 CR = 0.5e-12
6 CS = CH + CR # 15.925 pF
7 a1 = CH / CS # 約 0.9686
8
9 f_LO = 2.4e9 # LO freq
10 N = 8
11 T_int = N / f_LO # 積分區間
12 f = np.logspace(1, 11, 1000) # 10 Hz ~ 100 GHz
13 w = 2*np.pi*f
14
15 # Part 1: 連續積分(不放電) ×  $\frac{1}{j\omega}$ 
16 # 有限窗積分(會放電) ×  $(1 - e^{-j\omega T_{int}})$ 
17 Hw_part = a1 * (1/(1j*w)) + (1-a1)*((1 - np.exp(-1j*w*T_int)) / (1j*w))
18
19 # Part 2: 再乘上 ZOH
20 Hw_zoh = (1 - np.exp(-1j*w*T_int)) / (1j*w*T_int)
21
22 # 合併
23 H_new = (1/CS)*Hw_part * Hw_zoh
24
25 # Magnitude in dB
26 H_new_mag_dB = 20*np.log10(np.abs(H_new))
```

Q3-a

```
lab3-3-a.py > ...
1 import numpy as np
2 import matplotlib.pyplot as plt
3
4 # --- 參數設定 ---
5 C_R = 1e-12 # 單顆電容值 (假設四顆相同)
6 f_LO = 2.4e9 # LO 頻率
7 N = 8
8 T_int = N / f_LO # 積分時間
9
10 # --- 頻率軸 ---
11 f_min, f_max = 1e6, 1e10 # 1 MHz ~ 10 GHz
12 num_points = 2000
13 f = np.logspace(np.log10(f_min), np.log10(f_max), num_points)
14 w = 2 * np.pi * f
15
16 # --- (a) Integrate & Dump 傳遞函式 ---
17 Hw_num = (1 - np.exp(-1j * w * T_int)) # 分子 1 - e^{-j \omega T_{int}}
18 Hw_int = Hw_num / (1j * w) # 有限窗積分
19 Hw_hold = Hw_num / (1j * w * T_int) # 零階保持(ZOH)
20 H_a = (1 / C_R) * Hw_int * Hw_hold # 乘上 1/C
21
22 # --- 轉成 dB ---
23 H_a_mag_dB = 20*np.log10(np.abs(H_a))
```

Q3-b

```
lab3-3-b.py > ...
1 import numpy as np
2 import matplotlib.pyplot as plt
3
4 # --- 參數設定 ---
5 C_R = 1e-12
6 f_LO = 2.4e9
7 N = 8
8 T_int = N / f_LO
9
10 f_min, f_max = 1e6, 1e10
11 f = np.logspace(np.log10(f_min), np.log10(f_max), 2000)
12 w = 2 * np.pi * f
13
14 # (b) Continuous Integration # 1/(j \omega)
15 Hw_b_int = 1 / (1j * w)
16 Hw_b_hold = (1 - np.exp(-1j * w * T_int)) / (1j * w * T_int)
17 H_b = (1 / C_R) * Hw_b_int * Hw_b_hold
18
19 H_b_mag_dB = 20*np.log10(np.abs(H_b))
```

Q3-c

```
lab3-3-c.py > ...
1 import numpy as np
2 import matplotlib.pyplot as plt
3
4 # --- 1. 參數 ---
5 C_R_list = [2e-12, 3e-12, 4e-12, 6e-12] # 不同大小的放電電容
6 C_sum = sum(C_R_list)
7
8 f_L0 = 2.4e9
9 N = 8
10 T_int = N / f_L0
11
12 # --- 2. 頻率軸 ---
13 f_min, f_max = 1e6, 1e10
14 num_points = 2000
15 f = np.logspace(np.log10(f_min), np.log10(f_max), num_points)
16 w = 2 * np.pi * f
17
18 # --- 3. F(f) = [ (1 - e^{-jwT_int}) / (j w) ] * [ (1 - e^{-jwT_int}) / (j w T_int) ]
19 Hw_num = (1 - np.exp(-1j * w * T_int))
20 Ff = (Hw_num / (1j * w)) * (Hw_num / (1j * w * T_int))
21
22 # --- 4. H_c(f) = [ 4 * F(f) ] / sum_i C_Ri
23 # (同時開窗積分，最後並聯輸出)
24 H_c = (len(C_R_list) * Ff) / C_sum
25
26 # --- 轉 dB ---
27 H_c_mag_db = 20 * np.log10(np.abs(H_c))
```